

RECTIFIERS


Rectifier

- ❖ The process by which an alternating current (or voltage) is transformed into a direct current (or voltage) is called **rectification**.
- ❖ The device which converts alternating current (or voltage) into direct current (or voltage) is called a **rectifier**.
- ❖ Rectifiers may be made of **solid state diodes, vacuum tube diodes**, mercury arc valves, and other components.
- ❖ Before the development of silicon semiconductor rectifiers, vacuum tube diodes and copper(I) oxide or selenium rectifier stacks were used.


Block Diagram of a Rectifier



Types Of Rectifier

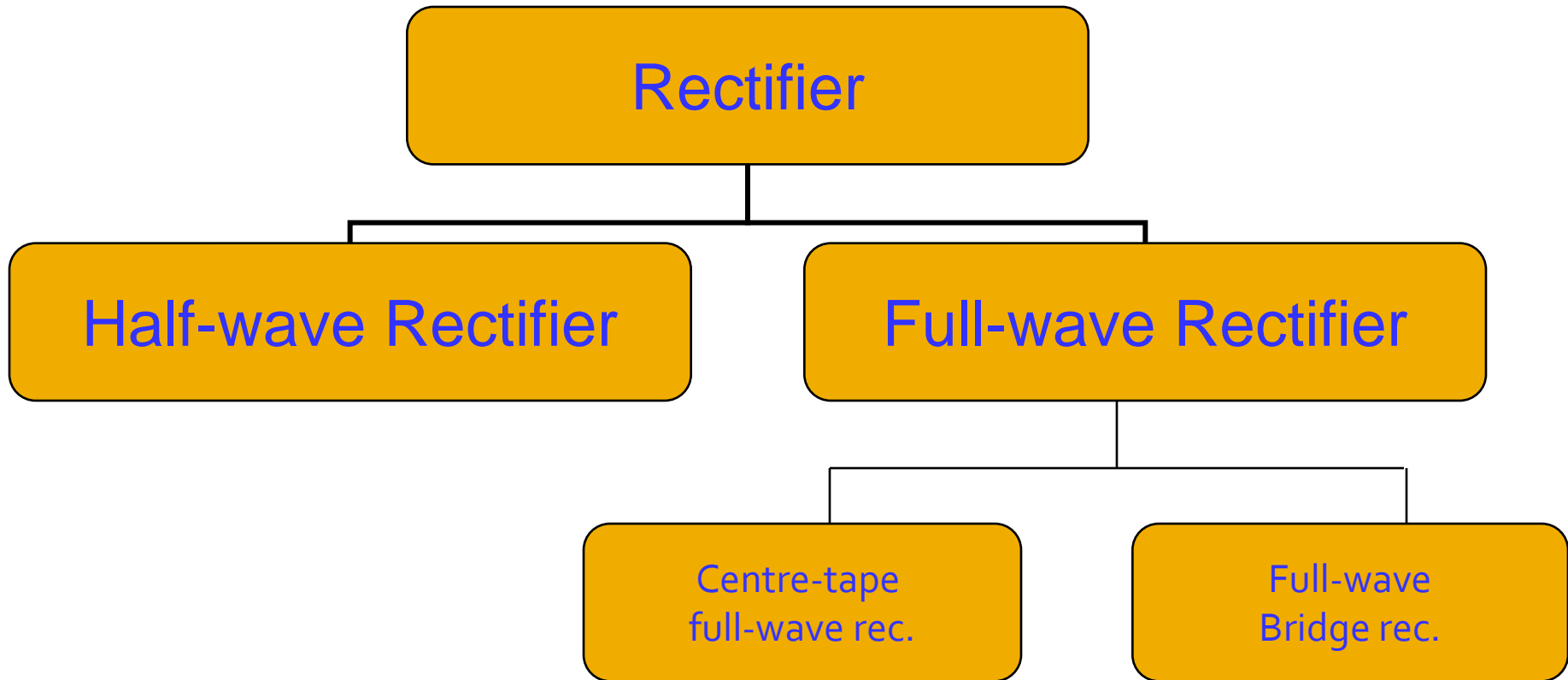

Half Wave Rectifier

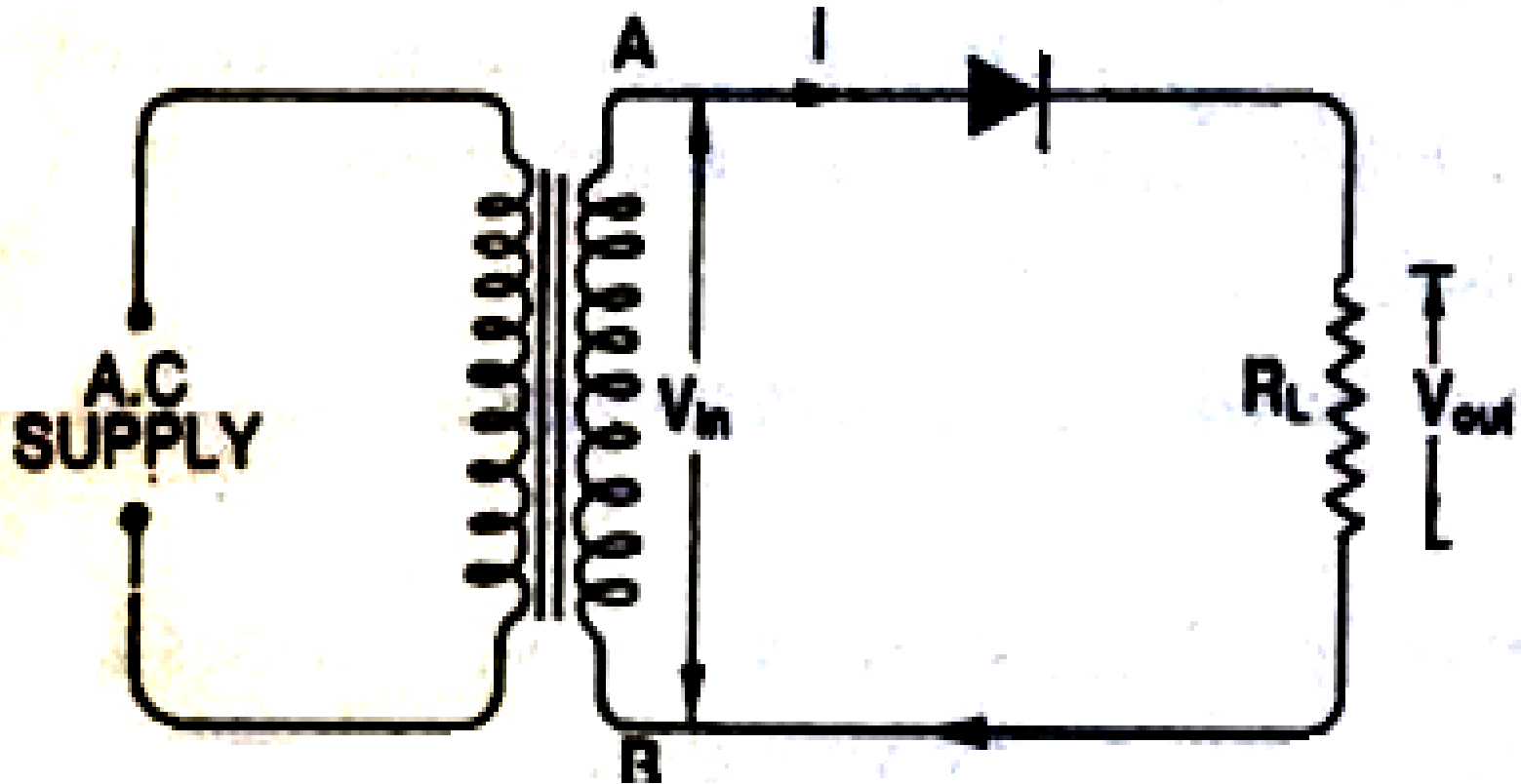


Circuit diagram


Half Wave Rectification

WORKING

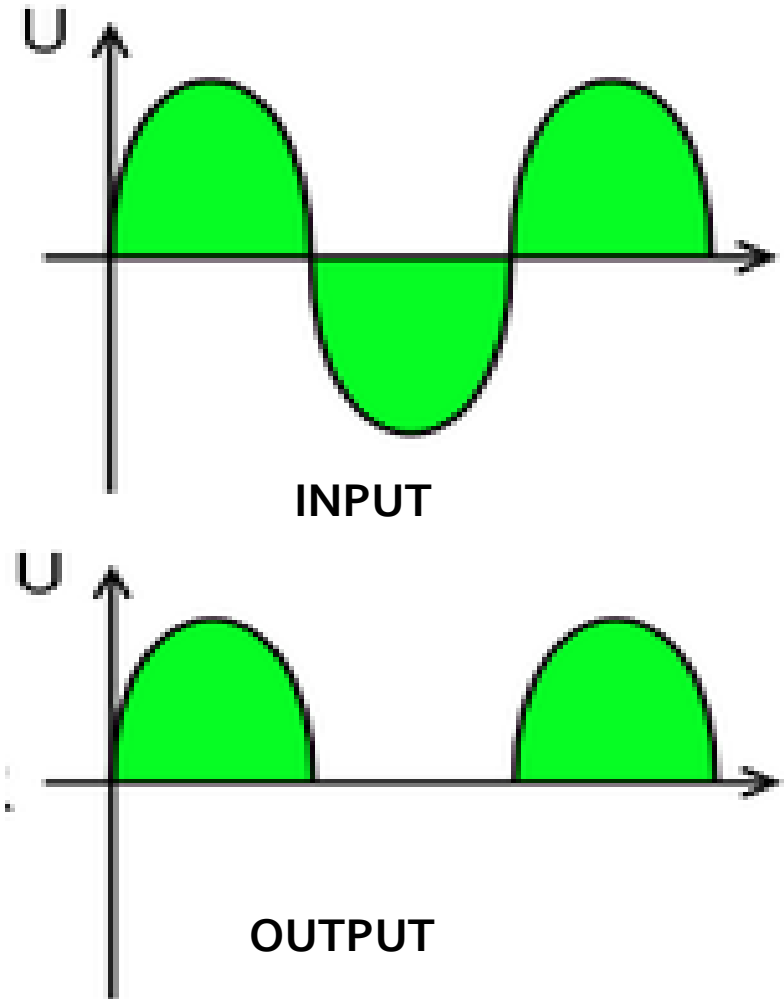- ❖ It uses a diode in series with a load resistance.
- ❖ The diode is conducting i.e. it is forward biased only for the positive half cycle of the input signal.
- ❖ Thus it provides output for only one half cycle of the input signal.
- ❖ For the other half cycle of the input the diode is reversed biased i.e. open-circuited and thus zero output is provided.



Full Wave Rectifier

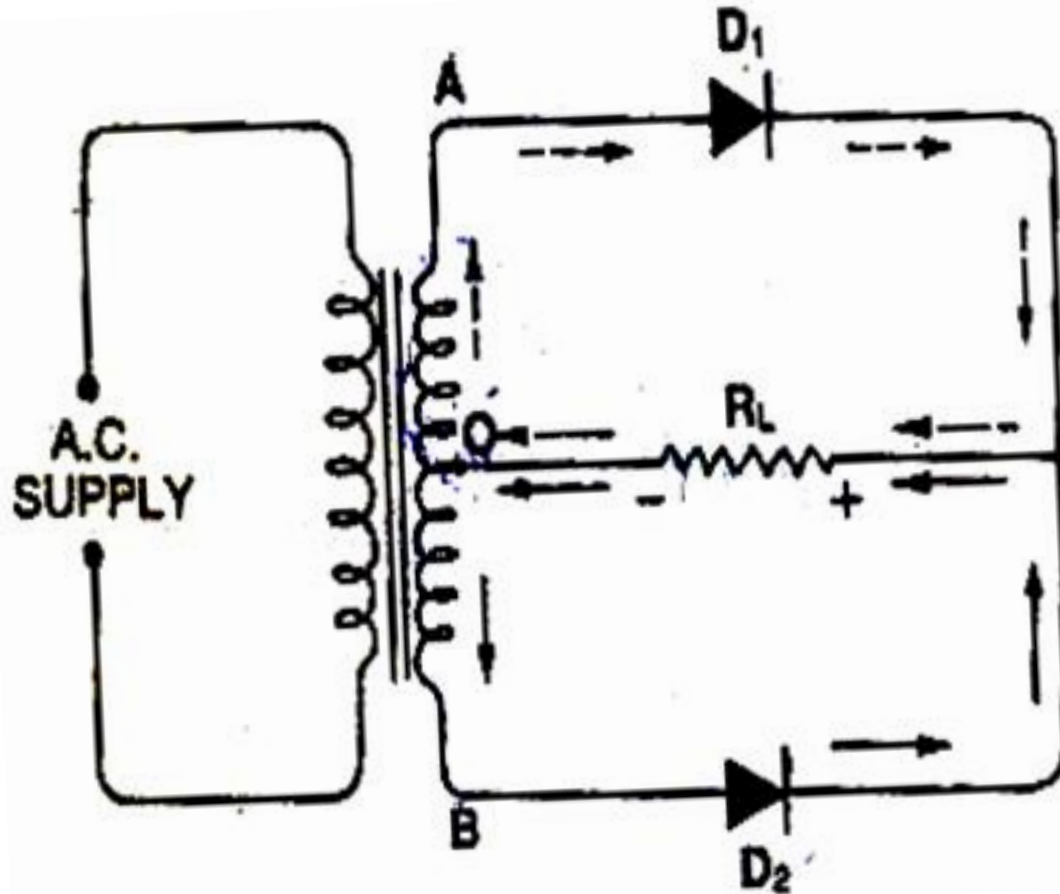


Circuit diagram


Full Wave Rectification

■ WORKING

- ❖ A center-tap full wave rectifier uses only two diodes but a center-tapped (CT) transformer to establish the input signal across each section of the transformer.
- ❖ During the positive half cycle of the input, applied to the primary of transformer D_1 will be forward biased assuming short-circuit equivalent and D_2 will be reversed biased assuming open-circuit equivalent.
- ❖ Its advantage over half wave rectifier is that it provides output for both the positive and negative half cycles.

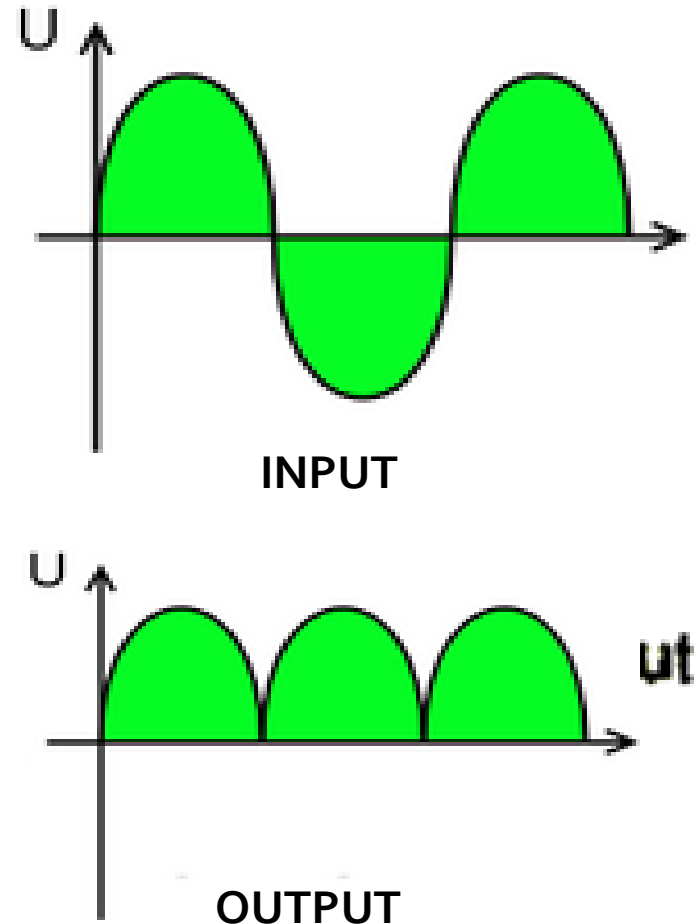

Bridge Rectifier

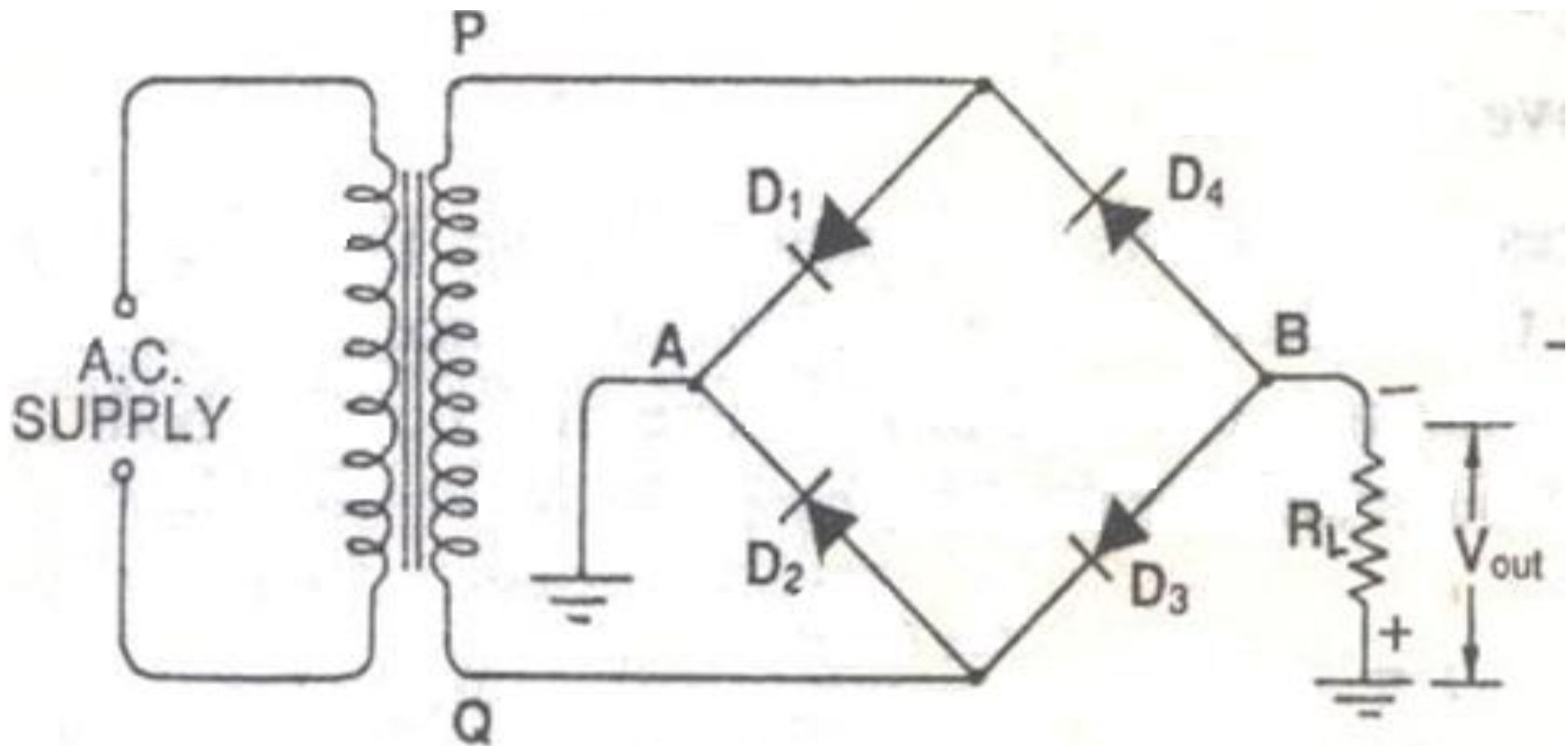


Circuit diagram


Working of Bridge Rectifier

■ WORKING

- ❖ A bridge rectifier uses four diodes for the process of rectification.
- ❖ Two diodes for each half cycle are conducting i.e. they are forward biased and the other two diodes for this half cycle are reversed biased i.e. they are non-conducting.
- ❖ For the positive half of the input the diodes D_2 and D_4 are forward biased and conducting while D_1 and D_3 are non-conducting. For the second half i.e. negative half of cycle the diodes D_1 and D_3 are conducting while D_2 and D_4 are reversed biased and non-conducting.

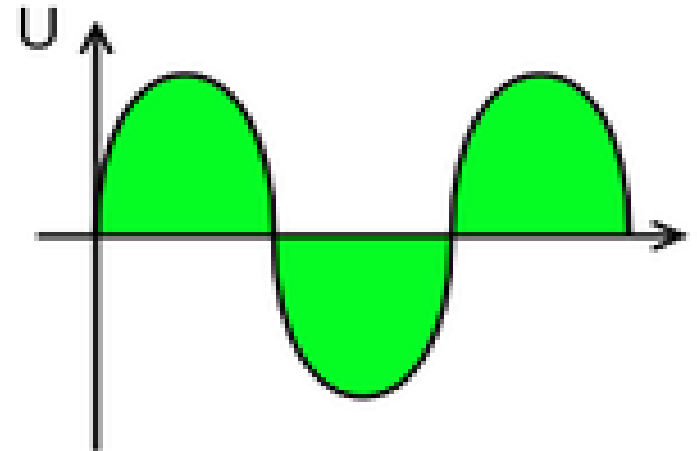

INPUT

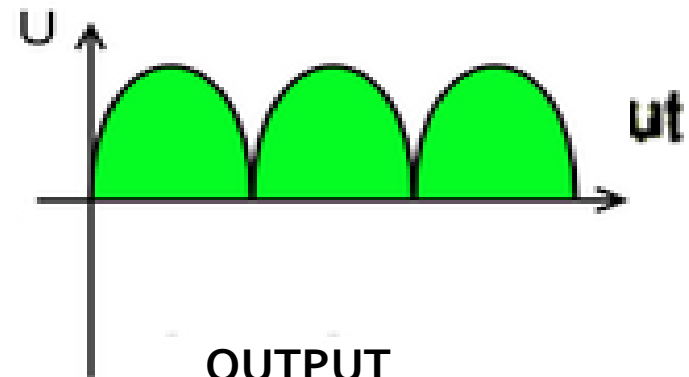

OUTPUT

Ripple Factor

$$\begin{aligned} \text{Ripple Factor (r)} &= \frac{\text{rms value of alternating component of load current (or voltage)}}{\text{average value of load current (or voltage)}} \\ &= \frac{I'_{\text{rms}}}{I_{\text{dc}}} = \frac{V'_{\text{rms}}}{V_{\text{dc}}} \end{aligned}$$

$$\begin{aligned} r &= \frac{(I_{\text{rms}}^2 - I_{\text{dc}}^2)^{1/2}}{I_{\text{dc}}} \\ &= \frac{(V_{\text{rms}}^2 - V_{\text{dc}}^2)^{1/2}}{V_{\text{dc}}} \end{aligned}$$

where

I_{rms} denotes the rms value of the total load voltage.
 I_{dc} is the average value of load current.

Rectification Efficiency

The efficiency of rectification is defined to be the ratio of the dc output power (P_{dc}) to the ac input power (P_i) of the rectifier. It is denoted by η and is usually expressed as a percentage

$$\begin{aligned}\eta &= \frac{P_{dc}}{P_i} \times 100 \% \\ &= \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_f + R_L)} \times 100\%\end{aligned}$$

Transformer Utilization Factor(TUF)

Transformer Utilization Factor is defined by

$$\text{TUF} = \frac{\text{dc power supplied to the load}}{\text{ac power rating of the transformer}} = \frac{P_{dc}}{P_{ac(\text{rated})}}$$

The Transformer Utilization Factor for

- ❖ A half wave rectifier is 0.287
- ❖ A full wave rectifier is 0.693
- ❖ A bridge rectifier is 0.812

COMPARISON OF RECTIFIERS

	HALF - WAVE	CENTER - TAP	BRIDGE TYPE
Number of diodes	1	2	4
Transformer necessary	NO	YES	NO
Maximum Efficiency	40.6%	81.2%	81.2%
Ripple Factor	0.48	1.21	1.21
rms value of output	$\frac{V_o}{2}$	$\frac{V_o}{\sqrt{2}}$	$\frac{V_o}{\sqrt{2}}$

Merits and Demerits of Bridge Rectifier


Merits

- ❖ It does not require a transformer.
- ❖ The peak inverse voltage (PIV) rating of a diode in a bridge rectifier is half that for a FWR, yielding same dc output.
- ❖ Bridge circuit is more compact and cheaper.
- ❖ The Transformer Utilization Factor(TUF) of a bridge rectifier is 0.812 compared to 0.693 of a full wave rectifier.

Demerits

- ❖ A full wave rectifier uses two diodes whereas Bridge rectifier uses four diodes.
- ❖ Since current flows in two diodes in series, large power is dissipated. Hence it is not suitable for low voltages.

FILTERS

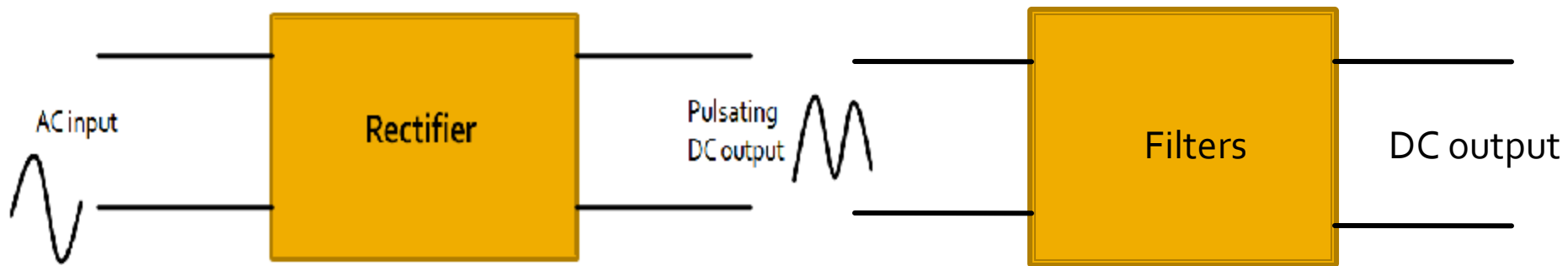

- ❖ The pulsating DC output of a rectifier is provided as input to the Filter circuit which provides a pure DC as output.
- ❖ The filter circuit generally consist of a combination of inductance and capacitance but in its simplest form this can be what is known as filter capacitor.
- ❖ A capacitor resists change in voltage and inductor resists change in current. This property of capacitor and inductor is used in a filter circuit.

Types Of Filters

There are basically four types of filters :

- ❖ C – Filter
- ❖ L – Filter
- ❖ LC – Filter
- ❖ CLC (or π) Filter

Applications Of Rectifiers

- ❖ The primary application of rectifiers is to derive DC power from an AC supply. Virtually all electronics except simple motor circuits such as fans require a DC supply but mains power is AC so rectifiers find uses inside the power supplies of virtually all electronic equipment.
- ❖ Rectifiers also find a use in detection of amplitude modulated radio signals. The signal may or may not be amplified before detection but if unamplified a very low voltage drop diode must be used.
- ❖ Rectifiers are also used to supply polarised voltage for welding.