

# **CHOPPER**

**By**

**Dr. Ananyo Bhattacharya**

**Assistant Professor**

**EE Department**

**NIT Jamshedpur**

# INTRODUCTION

Chopper is a static device.

A variable dc voltage is obtained from a constant dc voltage source.

Also known as dc-to-dc converter.

Widely used for **motor control**.

Also used in **regenerative braking**.

Thyristor converter offers greater efficiency, faster response, lower maintenance, smaller size and smooth control

# Definition of Chopper

A chopper is an electronic switch that is used to interrupt one signal under the control of another.

In other words we can say that, a chopper is a kind of switch which allows the power flow in the circuit for a required duration.

Thus, the chopper is also known as a d.c. to d.c converter.

# Types of Choppers


Step-down choppers:

In step down chopper **output voltage is less than input voltage.**

Step-up choppers:

In step up chopper **output voltage is more than input voltage.**

# Step-up chopper

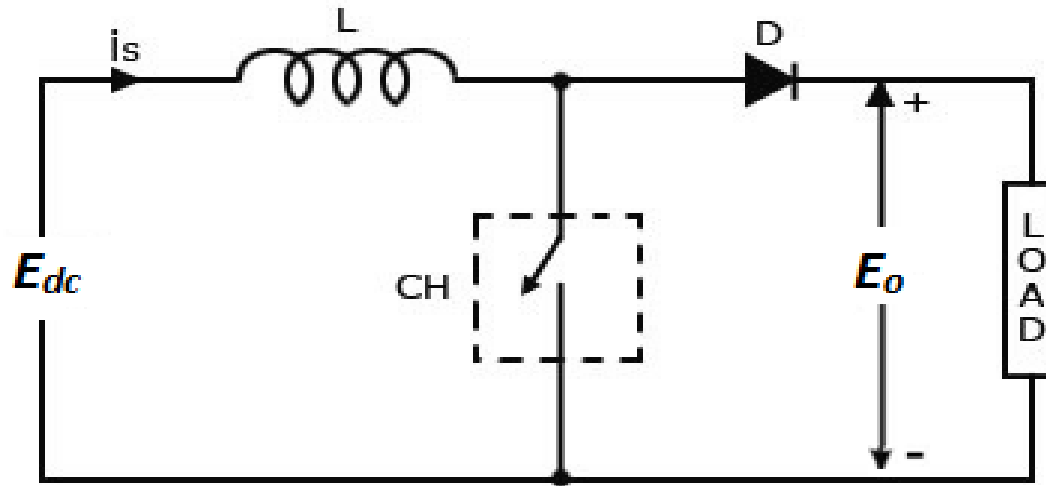

## Definition :

The chopper can be use to produced higher voltages at the load than the input voltage (i.e.,  $E_o \geq E_{dc}$ ). This is called as Step-up chopper

# Working


Case 1 : When the chopper is on the current  $I_L$  flows through inductor and it stores the energy during on period.

Case 2 : When the chopper is on the inductor force to permit the flow of current through the diode and the load. Therefore the load voltage becomes  $E_0 = E_{dc} + E_L$ .

$$E_0 = E_{dc} + L \cdot \frac{d}{dt} \cdot (I_L)$$

When the inductor current decreases to zero, the polarity across inductor gets reversed and the process is repeated.

# Step-Down chopper

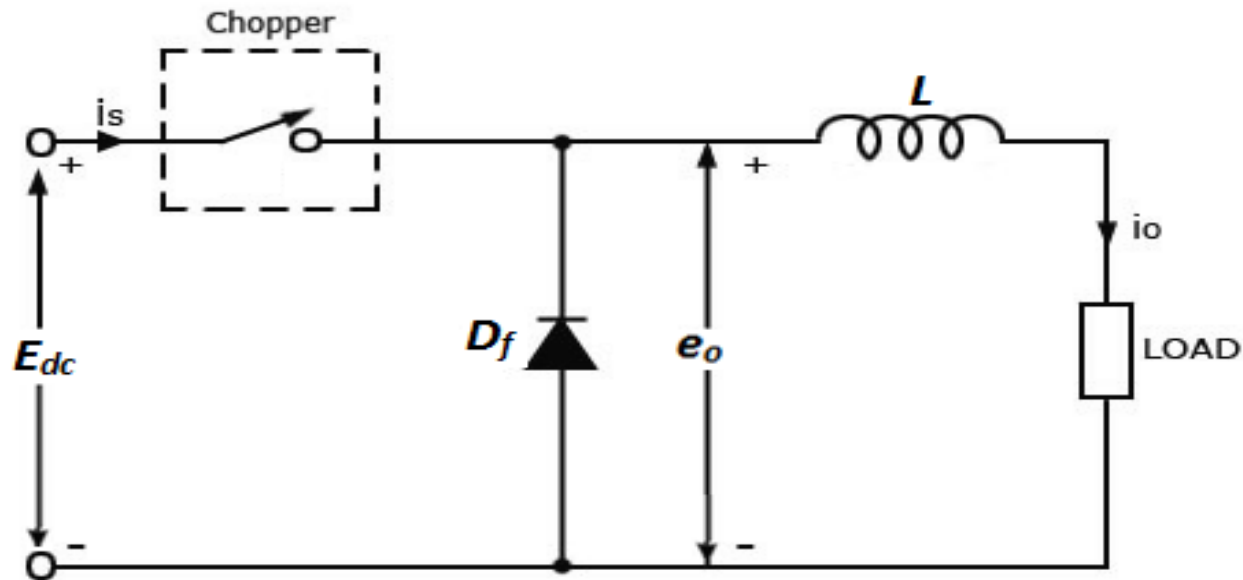

## Definition :

When the output voltage is less than the input dc voltage ( $E_0 < E_{dc}$ ) then it is called as Step-down copper.

$$\text{i.e., } E_0 < E_{dc}$$

## Working :

Case 1 : During the ON period of chopper the input voltage  $E_{dc}$  connected to the load and the inductor stores the energy across it.

Case2 : During the OFF period of chopper the inductor current and load current because of freewheeling diode get short circuited through the load and inductor. Therefore the load voltage is zero during the off period.



The output voltage  $E_0$  is expressed as,

$$E_0 = E_{dc} \times (T_{ON}) / (T_{ON} + T_{OFF}) \quad \dots(1)$$

Hence,

$$E_0 = E_{dc} (T_{ON} / T) \quad \dots(2)$$

Here,

$$T_{ON} + T_{OFF} = T = \text{Chopping Period}$$

$$T_{ON} = \text{ON period of chopper}$$

$$T_{OFF} = \text{OFF period of chopper}$$

$$\alpha = T_{ON} / T$$

The ratio of  $T_{ON} / T$  is called as duty cycle and represented as ' $\alpha$ '.

$$E_0 = E_{dc} \cdot \alpha$$

Where,


the chopping frequency control the output voltage.

$$E_0 = E_{dc} \cdot T_{ON} \cdot F$$

Where,

$$F = 1/T = \text{Chopping frequency}$$

# Chopper Configuration

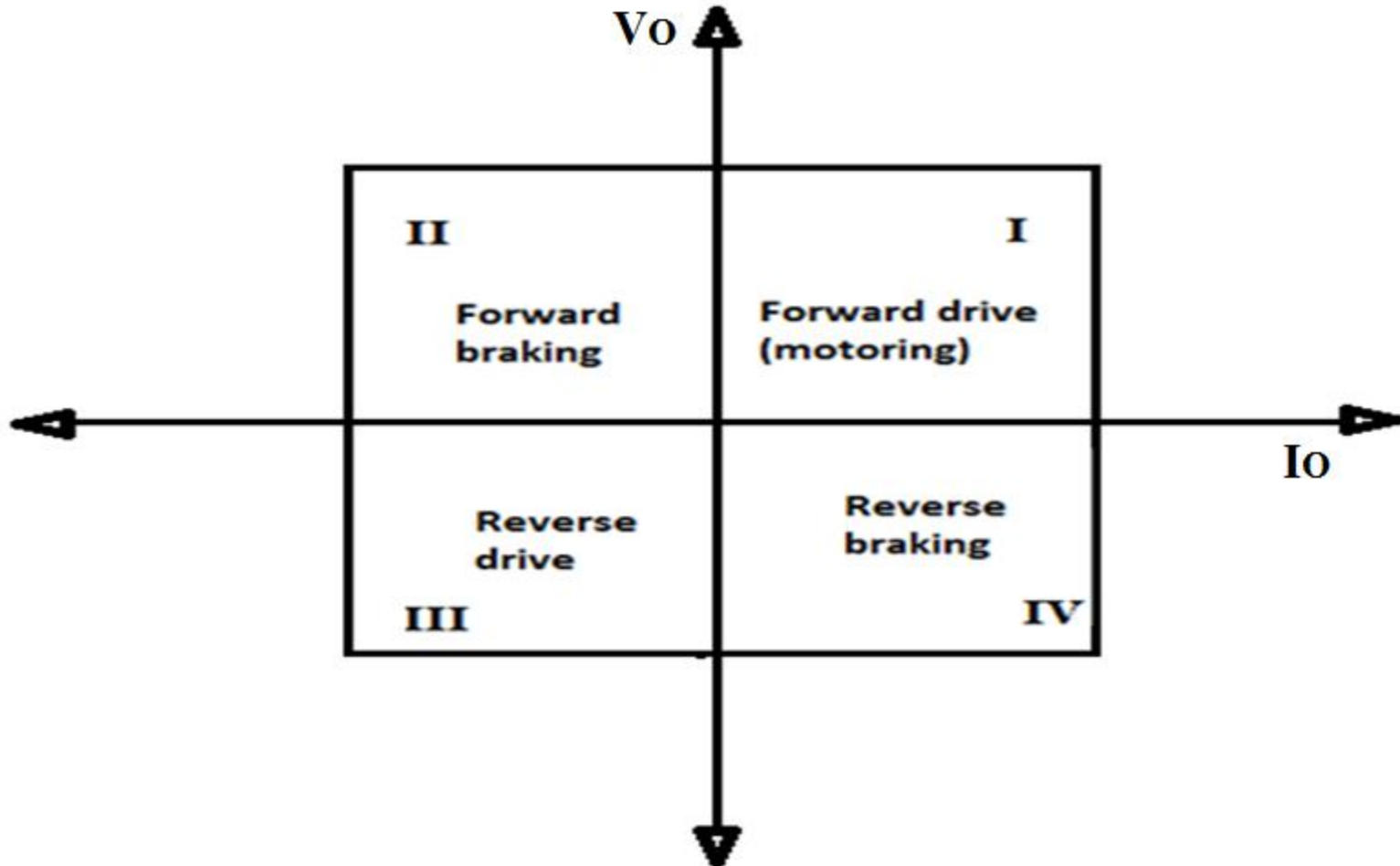

# Chopper Configuration

- Figure shows the quadrant based chopper classification according to the nature of voltage and current .
- The dc chopper circuit is the combination of all these quadrants , in which the dc motor has to be operated as a load.

In quadrant second and fourth, the direction of energy flow is reversed and the motor is used as a generator rather than drive (motor).


In quadrant first and third , the motor is used as a drive in clockwise and anticlockwise direction respectively.

# Classification Of Choppers

Choppers are classified as:

- Class A Chopper
- Class B Chopper
- Class C Chopper
- Class D Chopper
- Class E Chopper

# Class A Chopper

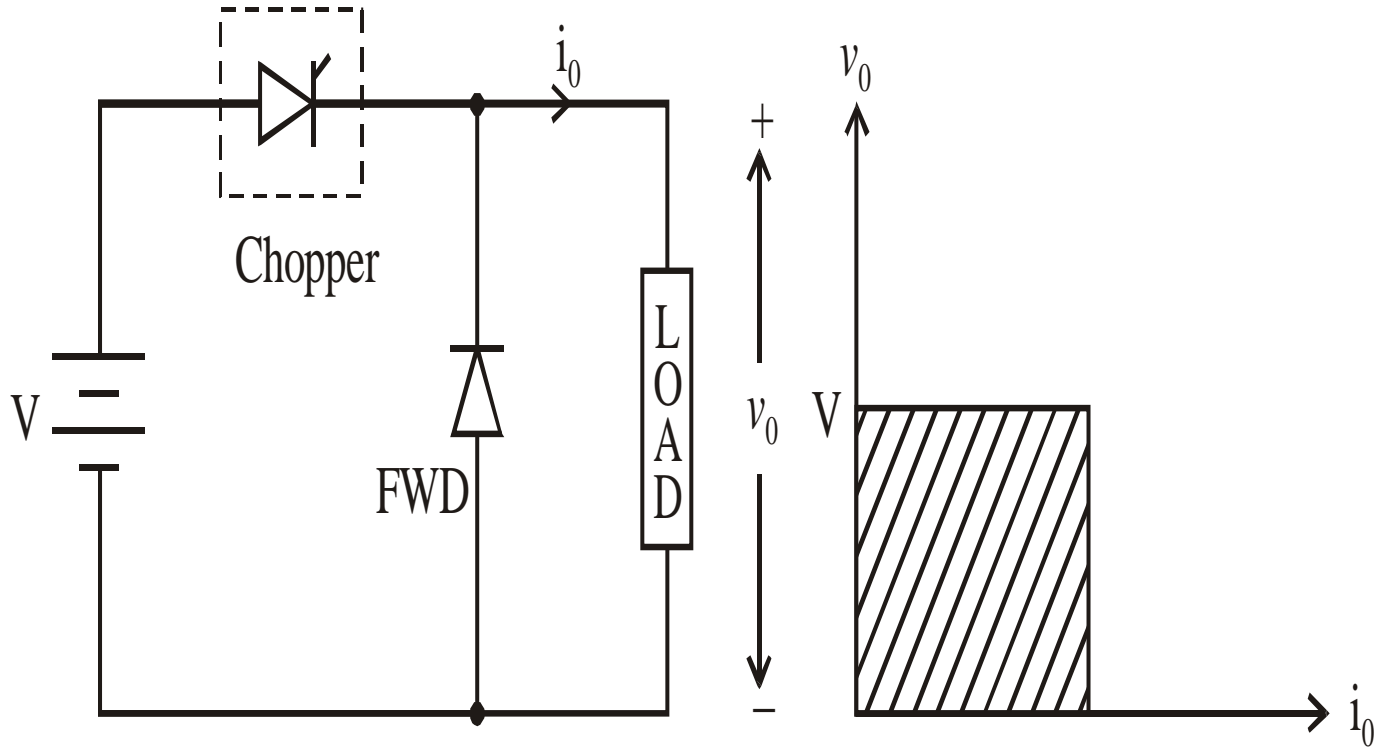

# Working

When chopper is ON, supply voltage  $V$  is connected across the load.

When chopper is OFF,  $v_o = 0$  and the load current continues to flow in the same direction through the FWD.

The average values of output voltage and current are always positive.

Class A Chopper is a first quadrant chopper


Class A Chopper is a step-down chopper in which power always flows from source to load.

It is used to control the speed of dc motor.


The output current equations obtained in step down chopper with  $R-L$  load can be used to study the performance of Class A Chopper.



# Waveforms

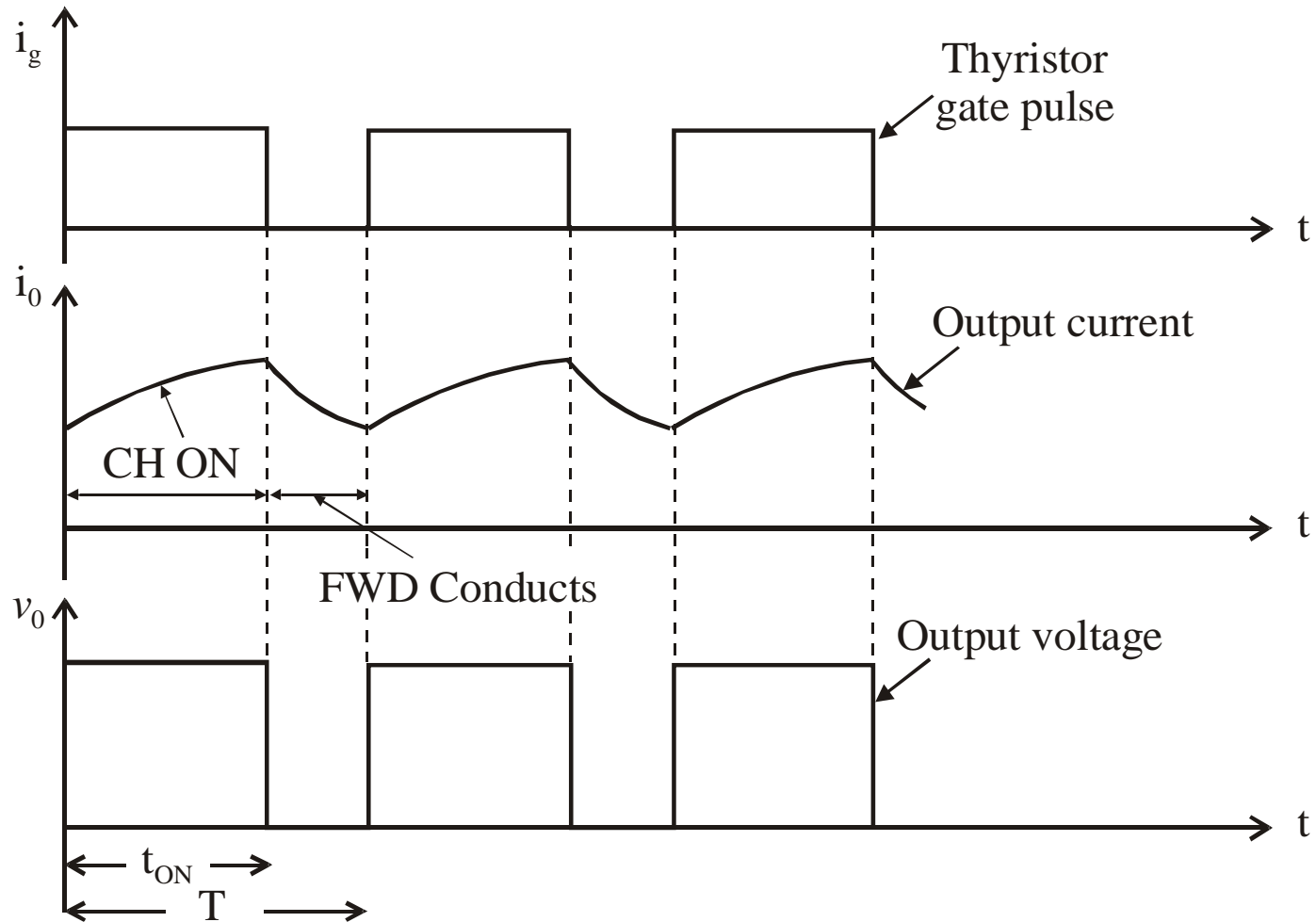

# Class B Chopper

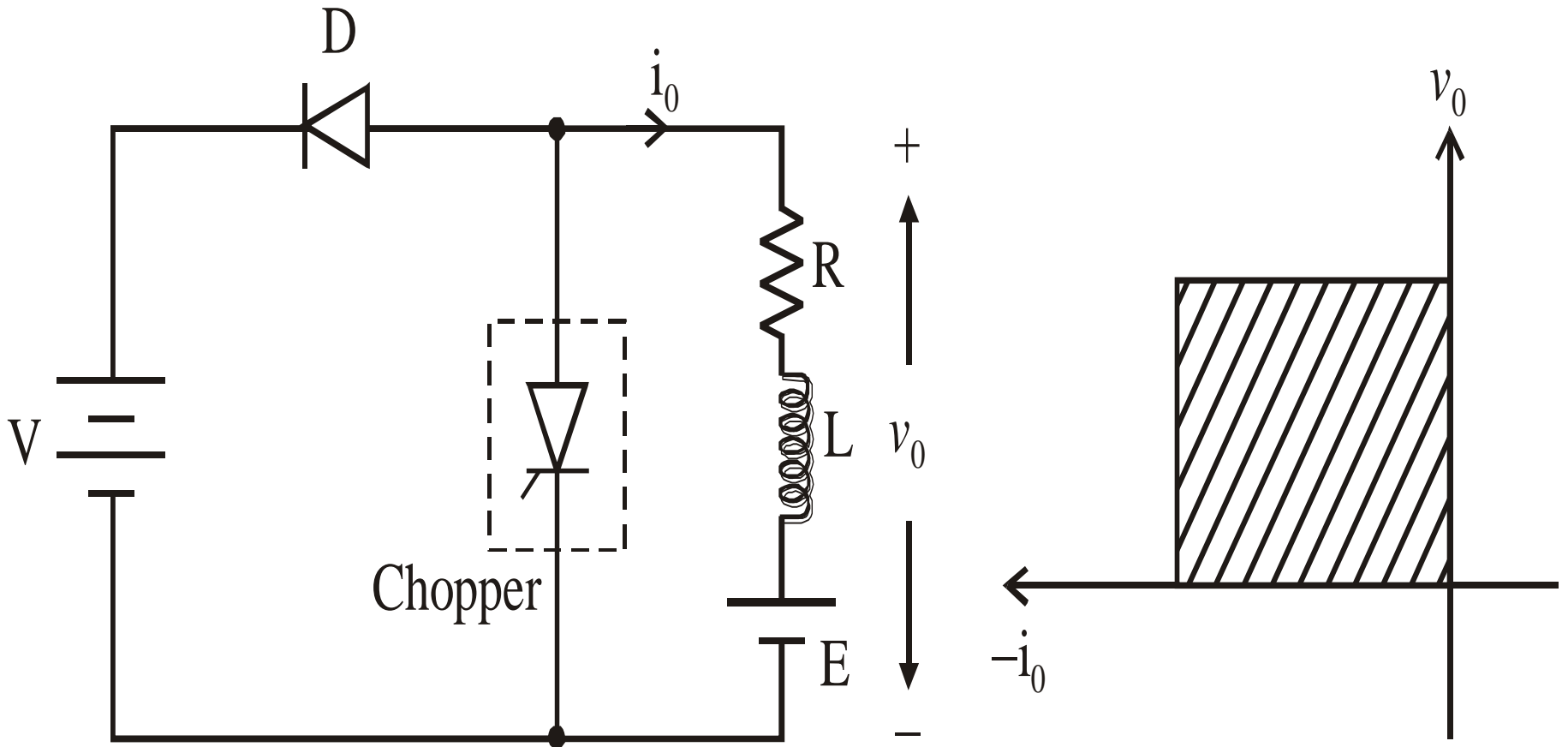

When chopper is ON,  $E$  drives a current through  $L$  and  $R$  in a direction opposite to that shown in figure.

During the ON period of the chopper, the inductance  $L$  stores energy.

When Chopper is OFF, diode  $D$  conducts, and part of the energy stored in inductor  $L$  is returned to the supply.

Average output voltage is positive.

Average output current is negative.


Therefore Class B Chopper operates in second quadrant.

In this chopper, power flows from load to source.


Class B Chopper is used for regenerative braking of dc motor.

Class B Chopper is a step-up chopper.

# Waveforms

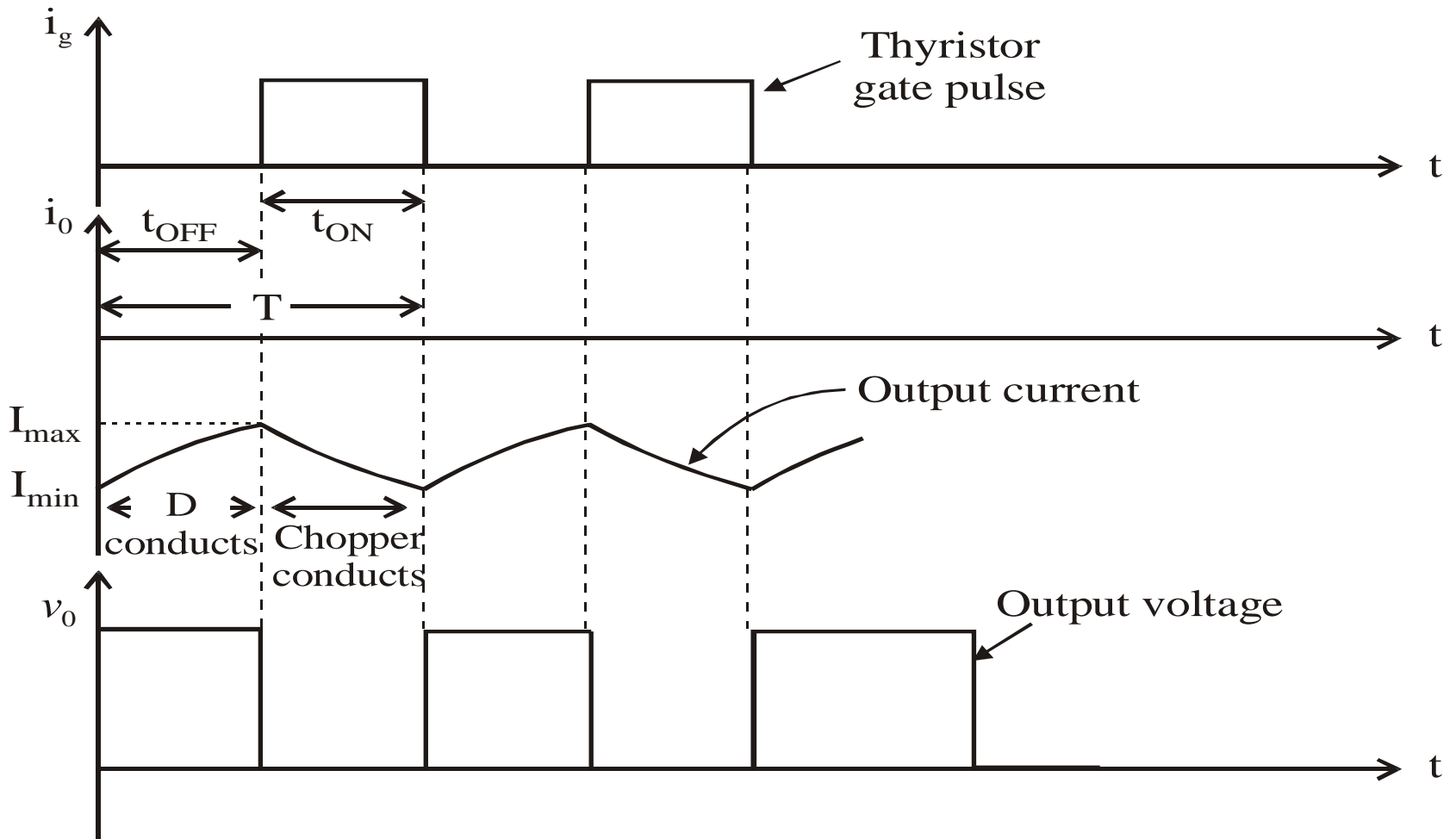

# Class C Chopper

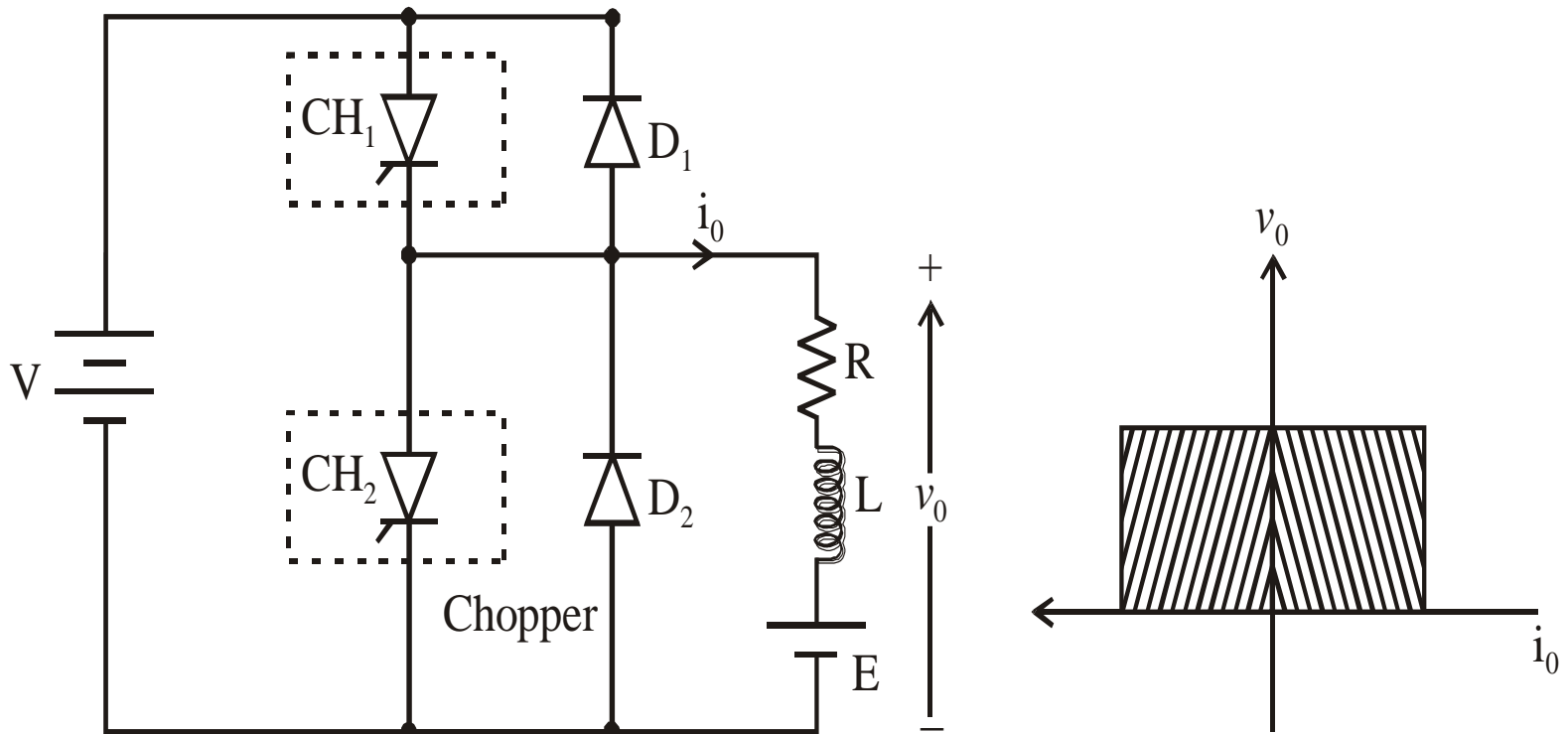

Class C Chopper is a combination of Class A and Class B Choppers.

For first quadrant operation,  $CH_1$  is ON or  $D_2$  conducts.

For second quadrant operation,  $CH_2$  is ON or  $D_1$  conducts.

When  $CH_1$  is ON, the load current is positive.

The output voltage is equal to ' $V$ ' & the load receives power from the source.

When  $CH_1$  is turned OFF, energy stored in inductance  $L$  forces current to flow through the diode  $D_2$  and the output voltage is zero.



Current continues to flow in positive direction.

When  $CH_2$  is triggered, the voltage  $E$  forces current to flow in opposite direction through L and  $CH_2$ .

The output voltage is zero.

On turning OFF  $CH_2$ , the energy stored in the inductance drives current through diode  $D_1$  and the supply.

Output voltage is  $V$ , the input current becomes negative and power flows from load to source.

Average output voltage is positive


Average output current can take both positive and negative values.

Choppers  $CH_1$  &  $CH_2$  should not be turned ON simultaneously as it would result in short circuiting the supply.


Class C Chopper can be used both for dc motor control and regenerative braking of dc motor.

Class C Chopper can be used as a step-up or step-down chopper.

# Waveforms

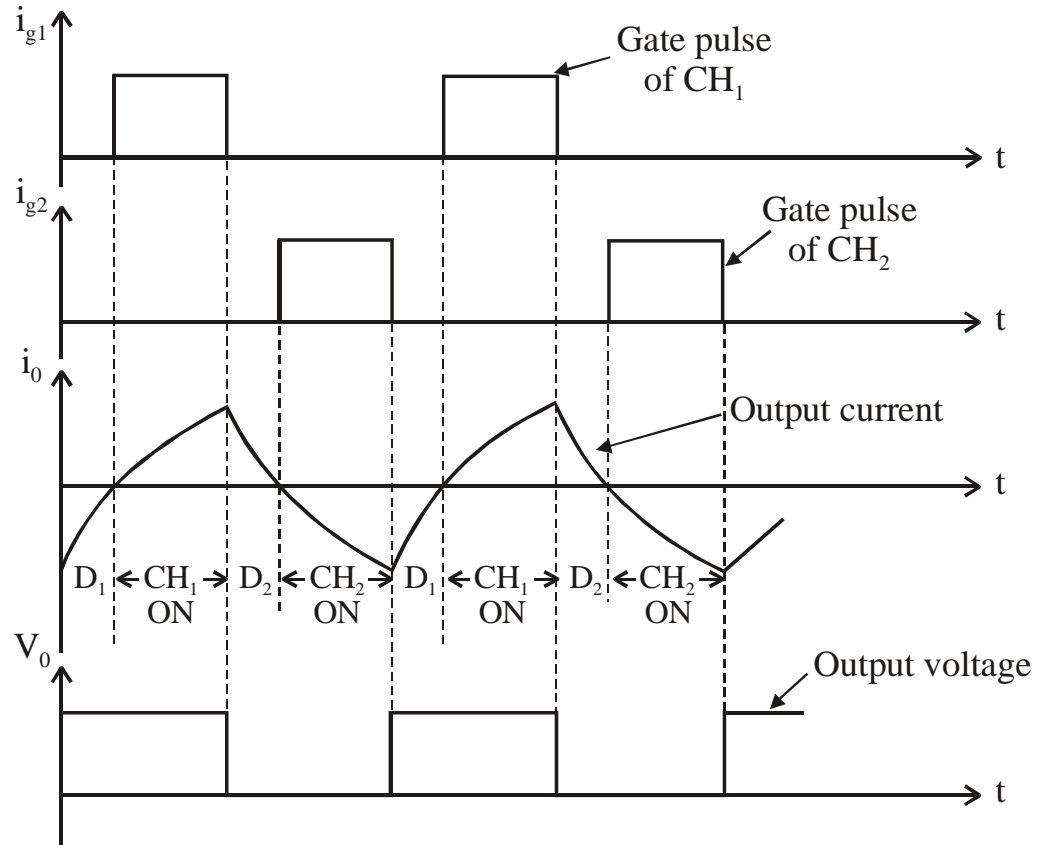

# Class D Chopper

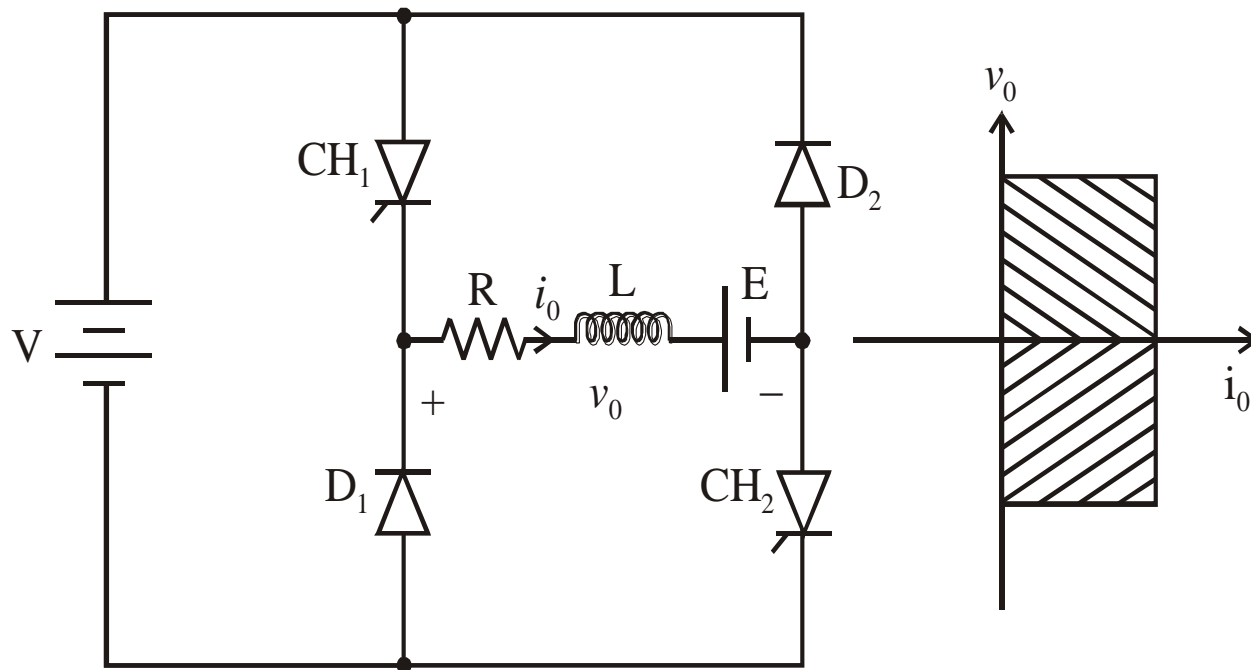

Class D is a two quadrant chopper.

When both  $CH_1$  and  $CH_2$  are triggered simultaneously, the output voltage  $v_o = V$  and output current flows through the load.

When  $CH_1$  and  $CH_2$  are turned OFF, the load current continues to flow in the same direction through load,  $D_1$  and  $D_2$ , due to the energy stored in the inductor L.


Output voltage  $v_o = -V$ .

Average load voltage is positive if chopper ON time is more than the OFF time


Average output voltage becomes negative if  $t_{ON} < t_{OFF}$

Hence the direction of load current is always positive but load voltage can be positive or negative.

# WAVEFORMS

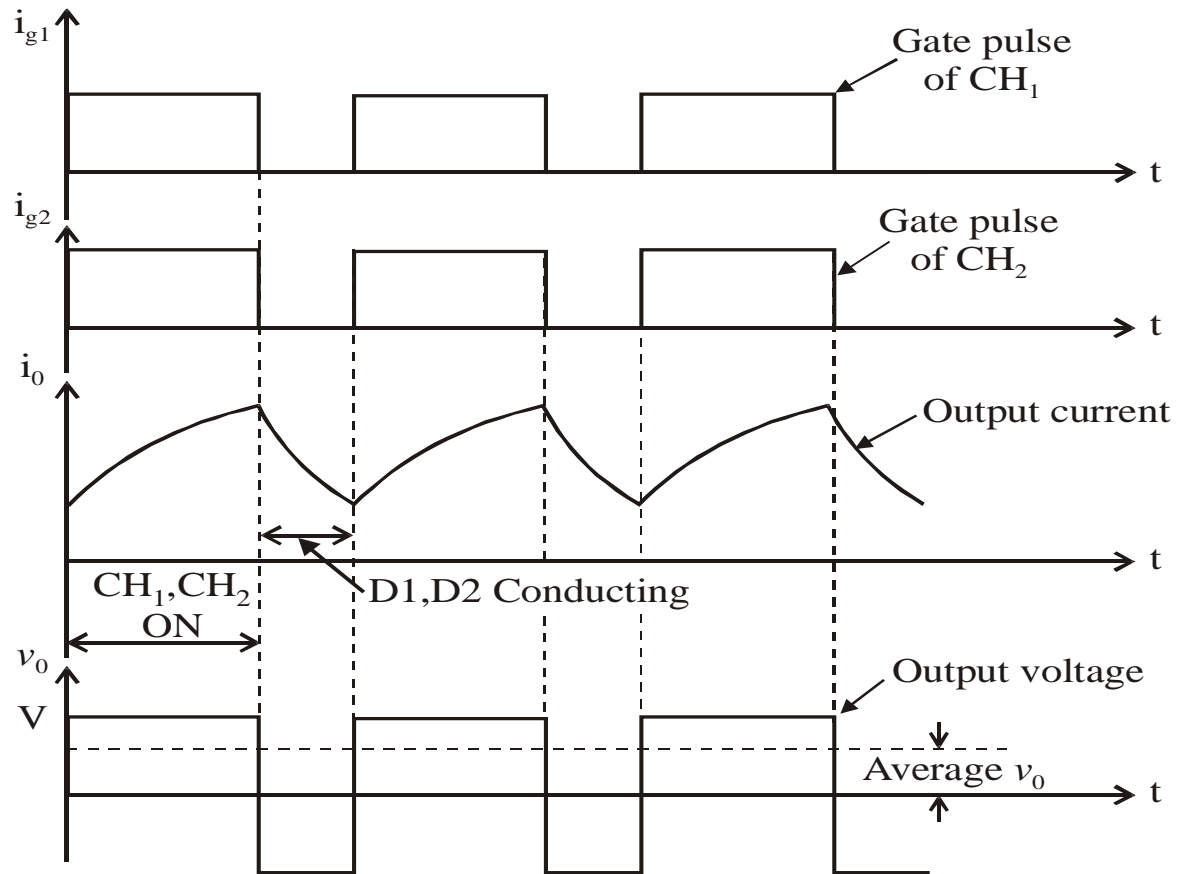


# Class E Chopper

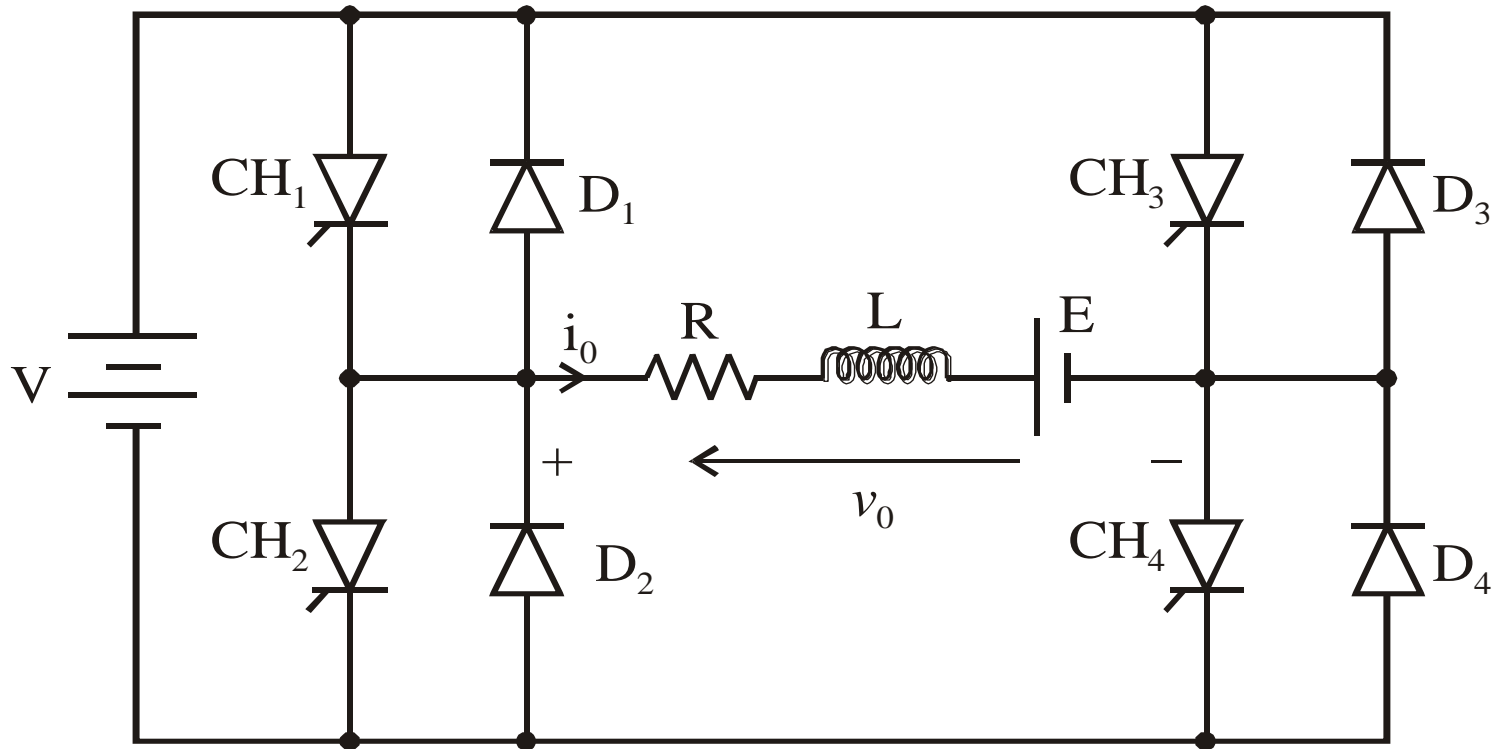



# Four Quadrant Operation

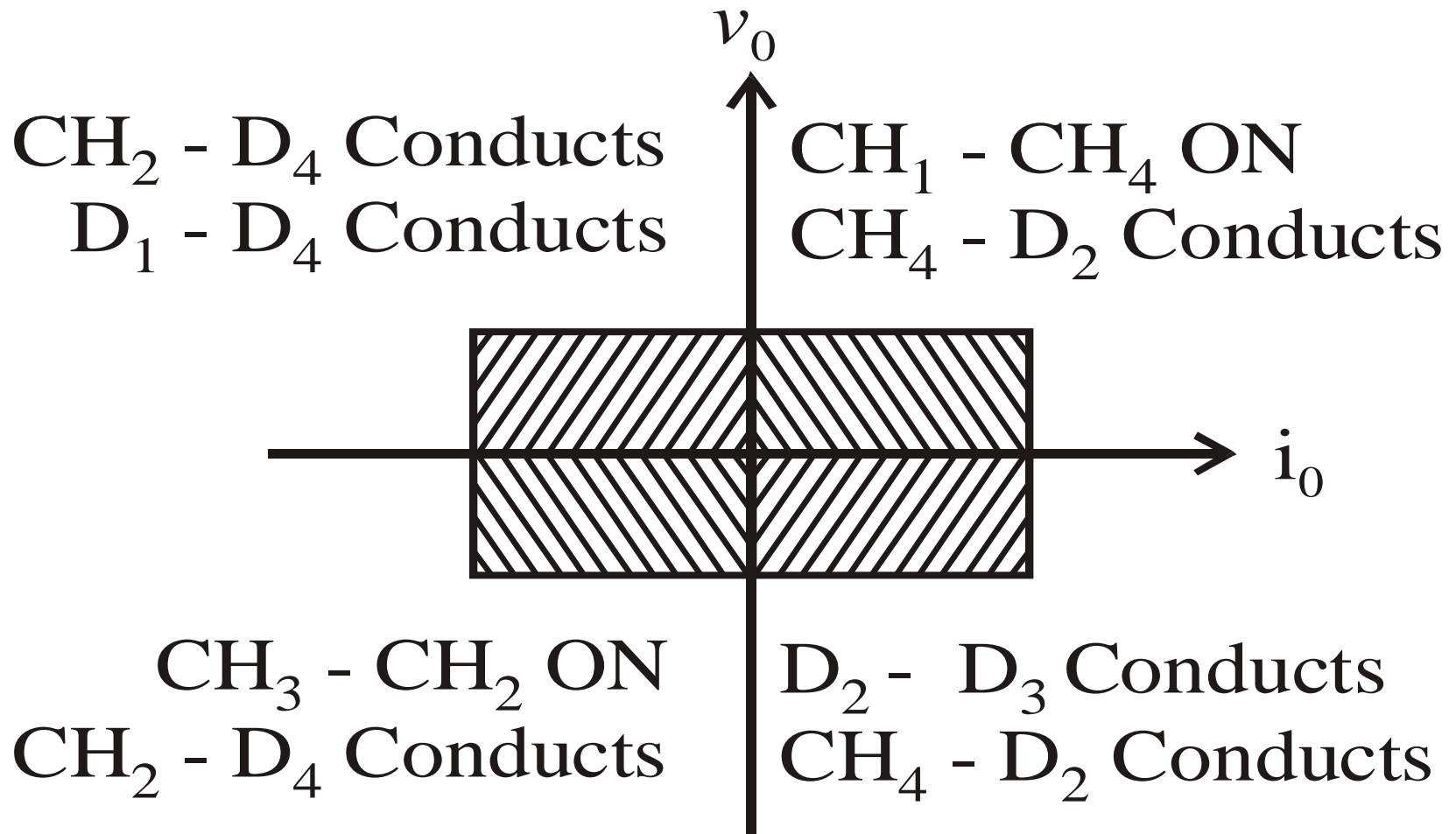

Class E is a four quadrant chopper

When  $CH_1$  and  $CH_4$  are triggered, output current  $i_o$  flows in positive direction through  $CH_1$  and  $CH_4$ , and with output voltage  $v_o = V$ .

This gives the first quadrant operation.

When both  $CH_1$  and  $CH_4$  are OFF, the energy stored in the inductor L drives  $i_o$  through  $D_2$  and  $D_3$  in the same direction, but output voltage  $v_o = -V$ .


Therefore the chopper operates in the fourth quadrant.

When  $CH_2$  and  $CH_3$  are triggered, the load current  $i_o$  flows in opposite direction & output voltage  $v_o = -V$ .

Since both  $i_o$  and  $v_o$  are negative, the chopper operates in third quadrant.

- When both  $CH_2$  and  $CH_3$  are OFF, the load current  $i_o$  continues to flow in the same direction  $D_1$  and  $D_4$  and the output voltage  $v_o = V$ .
- Therefore the chopper operates in second quadrant as  $v_o$  is positive but  $i_o$  is negative.

# Jones Chopper

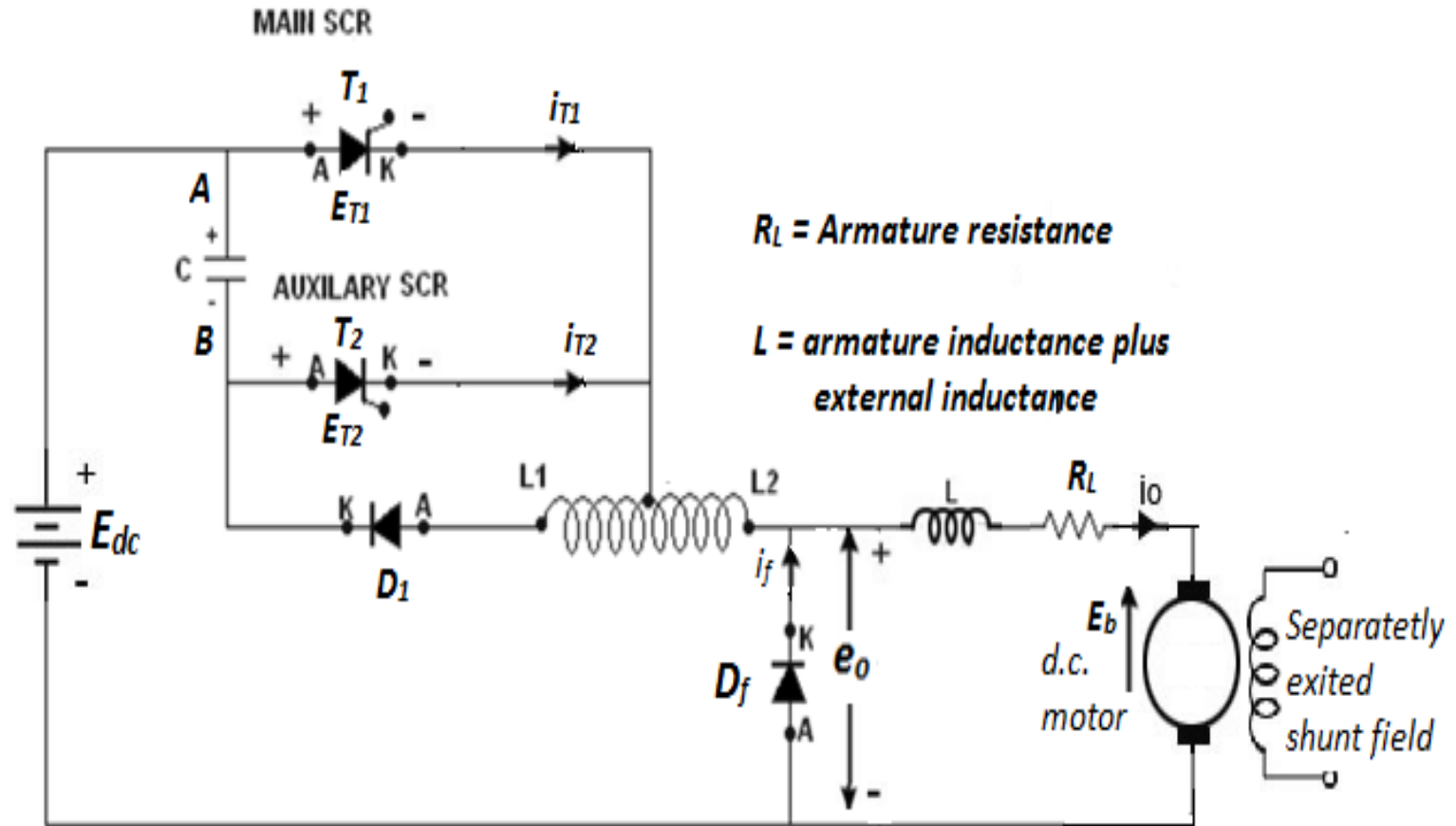

# Working :

- Figure shows the basic power circuit of Jones chopper. This chopper circuit is an example of Class D commutation. In this circuit, SCR  $T_1$  is the main thyristor, whereas SCR  $T_2$ , capacitor  $C$ ,  $D_2$ , and autotransformer (T) forms the commutating circuit for the main thyristor  $T_1$ .
- Therefore, the special features of this circuit is the tapped autotransformer T through a portion of which the load current flows. Here,  $L_1$  and  $L_2$  are closely coupled so that the capacitor always gets sufficient to turn off the main SCR  $T_1$ .

- If the main thyristor  $T_1$  is on for a long period , then the motor will reach the maximum steady-state speed determined by the battery voltage , the motor and the mechanical load characteristics. If thyristor  $T_1$  is off , the motor will not rotate. Now , if thyristor  $T_1$  is alternatively on and off in a cyclic manner , the motor will rotate at some speed between maximum and zero.
- Let us assume that initially capacitor C is charged to a voltage  $E_{dc}$  with the polarity shown in figure . As shown in fig. , SCR  $T_1$  is triggered at time  $t = t_1$  , current flows through the path  $C_A - T_1 - L_2 - C_B$  and capacitor C charges to opposite polarity , i.e. Plate B positive and plate A negative.

- However , diode  $D_1$  represents further oscillation of the resonating  $L_2 C$  circuit. Hence capacitor  $C$  retains its charge until SCR  $T_2$  is triggered. The capacitor voltage waveform are drawn at bottom plate B of capacitor.
- Now , at time  $t = t_3$  , SCR  $T_2$  is triggered. Current flow through the path  $C_B - T_2 - T_1 - C_A$  . Therefore, discharge of capacitor  $C$  reverse biases SCR  $T_1$  and turns it off. The capacitor again charges up with plate A positive and SCR  $T_2$  turns off because the current through it falls below the holding current value when capacitor  $C$  is recharged.



The cycle repeats when SCR  $T_1$  is again triggered. The use of autotransformer insures that whenever current is delivered from dc source to the load , a voltage is induced in  $L_2$  in the correct polarity for charging the commutating capacitor to a voltage higher than  $E_{dc}$  . Thus , the autotransformer measurably enhances the reliability of the circuit.

At  $t_5$  , the bottom plate (B) of capacitor C reaches a peak value. Since at  $t_5$  , the capacitor is charged to a voltage greater than  $E_{dc}$  , diode  $D_1$  is again forward biased . Capacitor C now discharges to a value lower than  $E_{dc}$  . The time duration  $t_3$  to  $t_4$  is the circuit turn off time presented to SCR  $T_1$ .

